
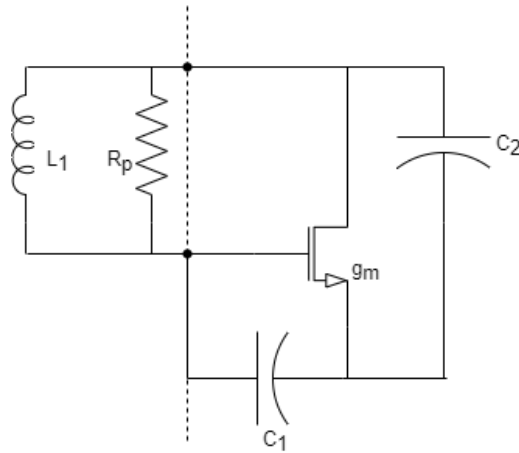


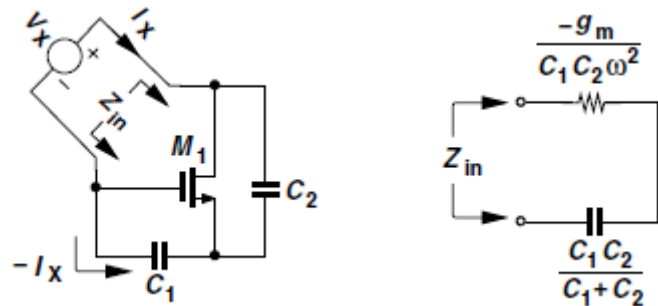Q1. For the given collpits oscillator, prove that the condition of oscillation is $g_m \cdot R_p = 4$ and $C_1 = C_2$ (3M)



Solution:




$$-\frac{I_X}{C_1 s} + V_X = \left(I_X + I_X \frac{g_m}{C_1 s} \right) \frac{1}{C_2 s}.$$

$$\frac{V_X(s)}{I_X} = \frac{1}{C_1 s} + \frac{1}{C_2 s} + \frac{g_m}{C_1 C_2 s^2}.$$

For a sinusoidal input, $s = j\omega$,
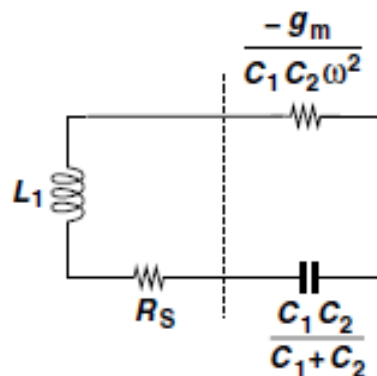
$$\frac{V_X(j\omega)}{I_X} = \frac{1}{jC_1 \omega} + \frac{1}{jC_2 \omega} - \frac{g_m}{C_1 C_2 \omega^2}.$$



It is simpler to model the loss of the inductor by a series resistance, R_S . The circuit oscillates if

$$R_S = \frac{g_m}{C_1 C_2 \omega^2}.$$

Under this condition, the circuit reduces to L_1 and the series combination of C_1 and C_2 , exhibiting an oscillation frequency of

$$\omega_{osc} = \frac{1}{\sqrt{L_1 \frac{C_1 C_2}{C_1 + C_2}}} \dots\dots\dots(1)$$

$$\frac{L_1 \omega}{R_S} \approx \frac{R_P}{L_1 \omega}$$


Thus,

$$\frac{L_1^2 \omega^2}{R_P} = \frac{g_m}{c_1 c_2 \omega^2}$$

Moreover, we can replace ω^2 with the value given in Eq.1, arriving at the startup condition:


$$g_m \cdot R_P = \frac{(c_1 + c_2)^2}{c_1 c_2} = \frac{c_1}{c_2} + \frac{c_2}{c_1} + 2 = 4 \text{ (Proved)}$$

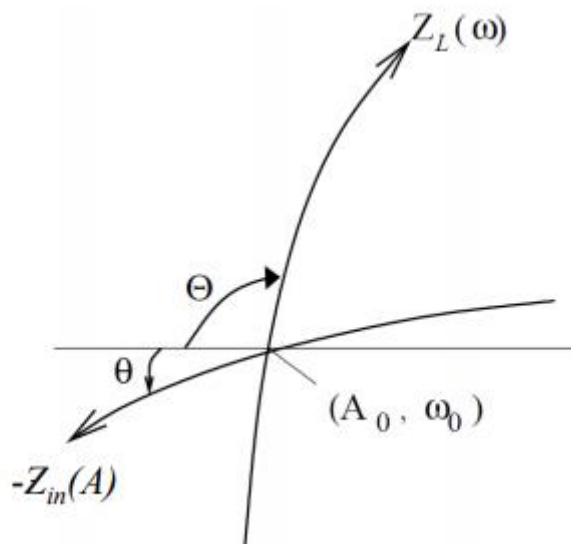Q2. For oscillation stability prove that $\Theta + \theta$ is between 0 and 180 degree. (give the fig of Z_L and Z_{in} and define what is Θ and θ) (3 M)




Solution:

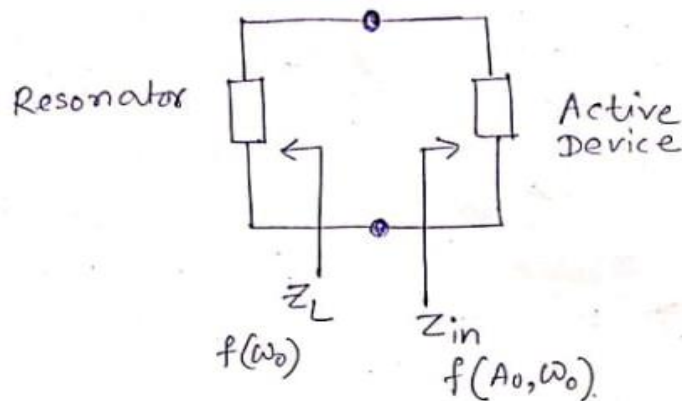Total oscillator circuit can be modelled into



This can be modelled as SFG:

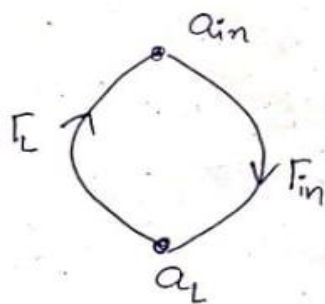

$a_{in}, a_L \rightarrow$ Normalised voltages & currents.

$$\frac{a_L}{a_{in}} = \frac{\Gamma_{in}}{1 - \Gamma_{in}\Gamma_L}$$

for oscillation, the TF must satisfy Barkhausen criteria

$$\Gamma_{in}\Gamma_L = 1$$

$$\Rightarrow \Gamma_{in}(A_0, \omega_0) = \frac{1}{\Gamma_L(\omega_0)}$$

$$\Rightarrow \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_L + Z_0}{Z_L - Z_0}$$


$$\Rightarrow Z_{in}(A_0, \omega_0) + Z_L(\omega_0) = 0$$

Now, Kurokawa has derived that for a stable oscillator,

$$\left[\frac{\partial R_{in}(A_0, \omega_0)}{\partial A} \frac{\partial X_L(\omega_0)}{\partial \omega} \right] - \left[\frac{\partial X_{in}(A_0, \omega_0)}{\partial A} \frac{\partial R_L(\omega_0)}{\partial \omega} \right] > 0$$

①

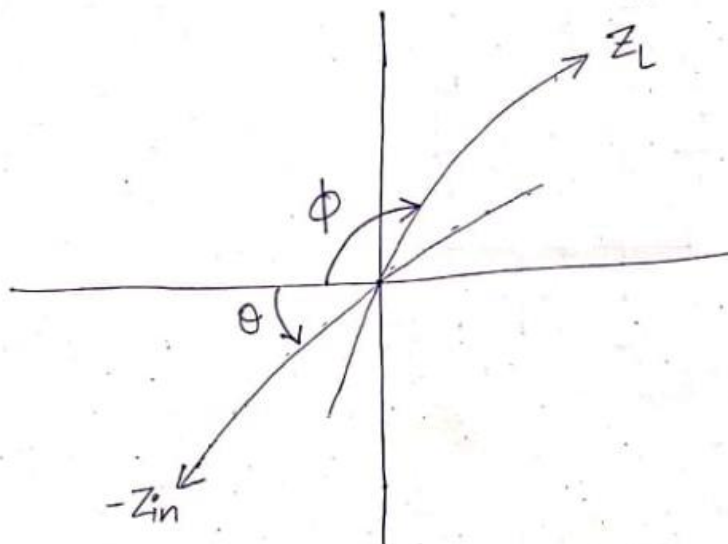where $R_{in} = \text{Re} \{Z_{in}\}$, $X_{in} = \text{Im} \{Z_{in}\}$
 $R_L = \text{Re} \{Z_L\}$, $X_L = \text{Im} \{Z_L\}$.



$$R_L = Z_L \cos (180 - \phi) = -Z_L \cos \phi$$

$$X_L = Z_L \sin (180 - \phi) = Z_L \sin \phi$$

$$-R_{in} = -Z_{in} \cos \theta \Rightarrow R_{in} = Z_{in} \cos \theta$$

$$-X_{in} = -Z_{in} \sin \theta \Rightarrow X_{in} = Z_{in} \sin \theta$$

Substituting into ①,

$$\frac{\partial}{\partial A} (Z_{in} \cos \theta) \cdot \frac{\partial}{\partial \omega} (Z_L \sin \phi) - \frac{\partial}{\partial A} (Z_{in} \sin \theta) \frac{\partial}{\partial \omega} (-Z_L \cos \phi) > 0$$


$$\Rightarrow [\cos \theta \sin \phi + \sin \theta \cos \phi] \left[2 \frac{\partial Z_{in}}{\partial A} \frac{\partial Z_L}{\partial \omega} \right] > 0$$

$$\Rightarrow \underbrace{2 \frac{\partial Z_{in}}{\partial A} \frac{\partial Z_L}{\partial \omega}}_{> 0 \text{ always}} \sin(\theta + \phi) > 0$$

$$\therefore \sin(\theta + \phi) > 0 \Rightarrow \boxed{0 < (\theta + \phi) < \pi}$$

(Proved)

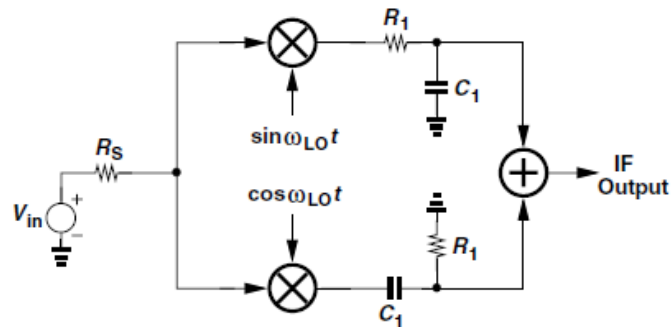Q3. The simplified Hartely architecture shown incorporates mixers having a voltage conversion gain of A_{mix} and infinite input impedance. Taking into account only the noise of the two resistors, compute the noise figure of the receiver with respect to a source resistance of R_S at an IF of $1/R_1C_1$. (3M)




Solution:


- $\text{Noise}_{\text{Out}} = 4KTR_1 * 2$
- Finding the gain:
 - For upper-branch: $A_{\text{mix}} * 0.5 * 0.5$
 - For bottom-branch: $A_{\text{mix}} * 0.5 * 0.5$
 - Total gain = $0.5 * A_{\text{mix}}$
- $\text{NF} = 1 + \frac{4KTR_1 * 2}{(0.5 * A_{\text{mix}})^2} * \frac{1}{4KTR_S} = 1 + \frac{8R_1}{R_S} \frac{1}{A_{\text{mix}}^2}$

Q4. In the given figure, find the voltage conversion gain (A_{VC}) of the mixer in dB. Assume that the resonant tank circuit (LRC) will sufficiently allow the $(\omega_{\text{RF}} - \omega_{\text{LO}})$ frequency component and reject others. Given, g_m of the MOSFETS is 2mS, $R=3\text{K}\Omega$, $V_{\text{bias}}=1\text{V}$, $V_{\text{thn}}=0.5\text{V}$, Amplitude of the square wave of LO=1.2V, (LO oscillated between 0 and 1.2 with frequency ω_{LO})

(3 M)

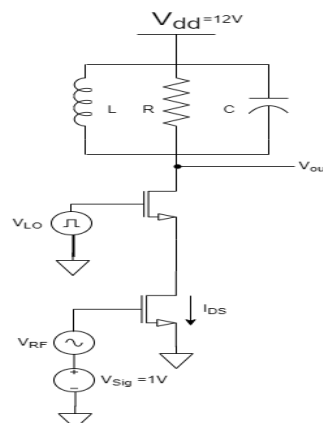

Solution:

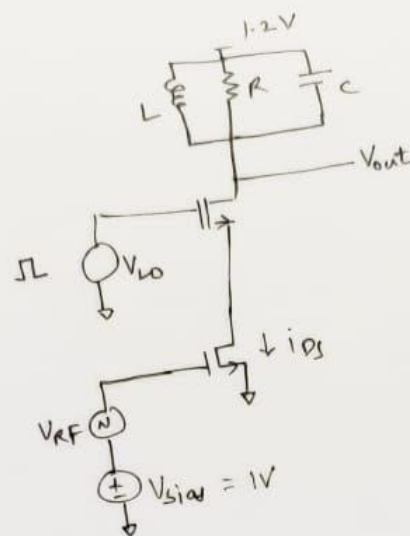

$$R = 3 \text{ k}\Omega$$

$$V_{th} = 0.5 \text{ V}$$

V_{Lo} = square wave toggling between 0 & 1 with frequency f_{Lo} , $A_{Lo} = 1.2 \text{ V}$

$$V_{RF} = V_{RF} \cos(\omega_{RF} t)$$

$$i_{Ds}(t) = \beta [V_{RF} \cos(\omega_{RF} t) + (V_{gs} - V_{th})]^2$$

$$= \beta [V_{RF}^2 \cos^2(\omega_{RF} t) + (V_{gs} - V_{th})^2 + 2V_{RF} (V_{gs} - V_{th}) \cos(\omega_{RF} t)]$$

$$\text{F-series of } Lo - \left[\frac{1}{2} + \frac{2}{\pi} \cos(\omega_{Lo} t) + \frac{2}{3\pi} \cos(3\omega_{Lo} t) + \dots \right] A_{Lo}$$

i_{Ds} flowing through Load -

$$A_{Lo} \beta [V_{RF}^2 \cos^2(\omega_{RF} t) + (V_{gs} - V_{th})^2 + 2V_{RF} (V_{gs} - V_{th}) \cos(\omega_{RF} t)] \cdot \left[\frac{1}{2} + \frac{2}{\pi} \cos(\omega_{Lo} t) + \dots \right]$$


since, the Tank is designed to pass only $\omega_{Lo} - \omega_{RF}$

$$\therefore 2V_{RF} (V_{gs} - V_{th}) \cos((\omega_{RF} - \omega_{Lo}) t) \cdot \frac{A_{Lo} \beta R}{\pi} = V_{out}$$

$$\therefore \text{Conversion gain} = \frac{A_{Lo} \beta}{\pi} \cdot \frac{2V_{RF} (V_{gs} - V_{th}) R}{V_{RF}} = \frac{A_{Lo}}{\pi} \times g_m R$$

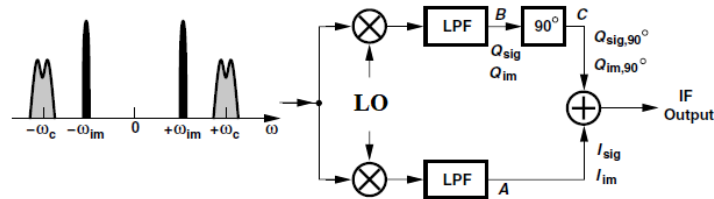Q5. For the given architecture, derive the expression of **Image Rejection Ratio (IRR)** as a function of ϵ and $\Delta\theta$. Hence prove that $IRR \approx \frac{4}{\epsilon^2 + \Delta\theta^2}$ if $\Delta\theta \ll 1\text{rad}$ and $\epsilon \ll 1\text{rad}$.

(Assume one LO waveform is expressed as $\sin\omega_{LO}t$ and the other as $(1+\epsilon)\cos(\omega_{LO}t + \Delta\theta)$ due to mismatches) **(4M)**



Solution:

$$x_A(t) = \frac{A_{sig}}{2} (1+\epsilon) \cos [(\omega_c - \omega_{Lo})t + \phi_{sig} + \Delta\theta] \\ + \frac{A_{im}}{2} (1+\epsilon) \cos [(\omega_{im} - \omega_{Lo})t + \phi_{im} + \Delta\theta]$$

$$x_{sig}(t) = \frac{A_{sig}}{2} (1+\epsilon) \cos [(\omega_c - \omega_{Lo})t + \phi_{sig} + \Delta\theta] \\ + \frac{A_{sig}}{2} \cos [(\omega_c - \omega_{Lo})t + \phi_{sig}]$$

$$x_{im}(t) = \frac{A_{im}}{2} (1+\epsilon) \cos [(\omega_{im} - \omega_{Lo})t + \phi_{im} + \Delta\theta] \\ - \frac{A_{im}}{2} \cos [(\omega_{im} - \omega_{Lo})t + \phi_{im}]$$

We know, avg. power of the vector sum $a \cos(\omega t + \alpha) + b \cos \omega t$ is $\frac{\tilde{a}^2 + 2ab \cos \alpha + b^2}{2}$.

$$\left. \frac{P_{im}}{P_{sig}} \right|_{out} = \frac{A_{im}^2}{A_{sig}^2} \frac{(1+\epsilon)^2 - 2(1+\epsilon) \cos \Delta\theta + 1}{(1+\epsilon)^2 + 2(1+\epsilon) \cos \Delta\theta + 1}$$

$$\therefore \boxed{IRR = \frac{(1+\epsilon)^2 + 2(1+\epsilon) \cos \Delta\theta + 1}{(1+\epsilon)^2 - 2(1+\epsilon) \cos \Delta\theta + 1}} \quad \text{--- (1)}$$

Since,
 $\cos \Delta\theta \approx 1 - \frac{\Delta\theta^2}{2}$ for $\Delta\theta \ll 1$ rad,


① is reduced to,

$$IRR \approx \frac{4 + 4\epsilon + \epsilon^2 - (1 + \epsilon)\Delta\theta^2}{\epsilon^2 + (1 + \epsilon)\Delta\theta^2}$$

In the numerator, the first term dominates and in the denominator $\epsilon \ll 1$ giving,


$$IRR \approx \frac{4}{\epsilon^2 + \Delta\theta^2}$$

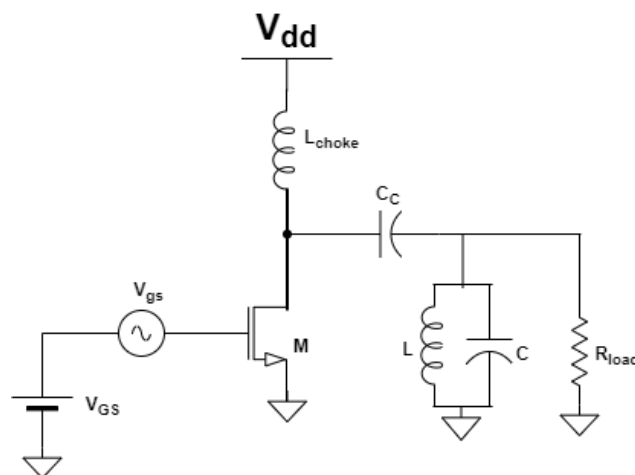Q6. Design a class-B RF power amplifier to deliver an output power of 4dBW at $f_0=2.45$ GHz. Assume $V_{DD}=1.8$ V, $V_{th}=0.6$ V (Threshold voltage of NMOS) $\mu_n C_{ox}=120\mu A/V^2$. Tabulate the values of R_{load} , L , C , W/L of transistor M. (6M)



Solution:

Waveforms at V_o and I_D -

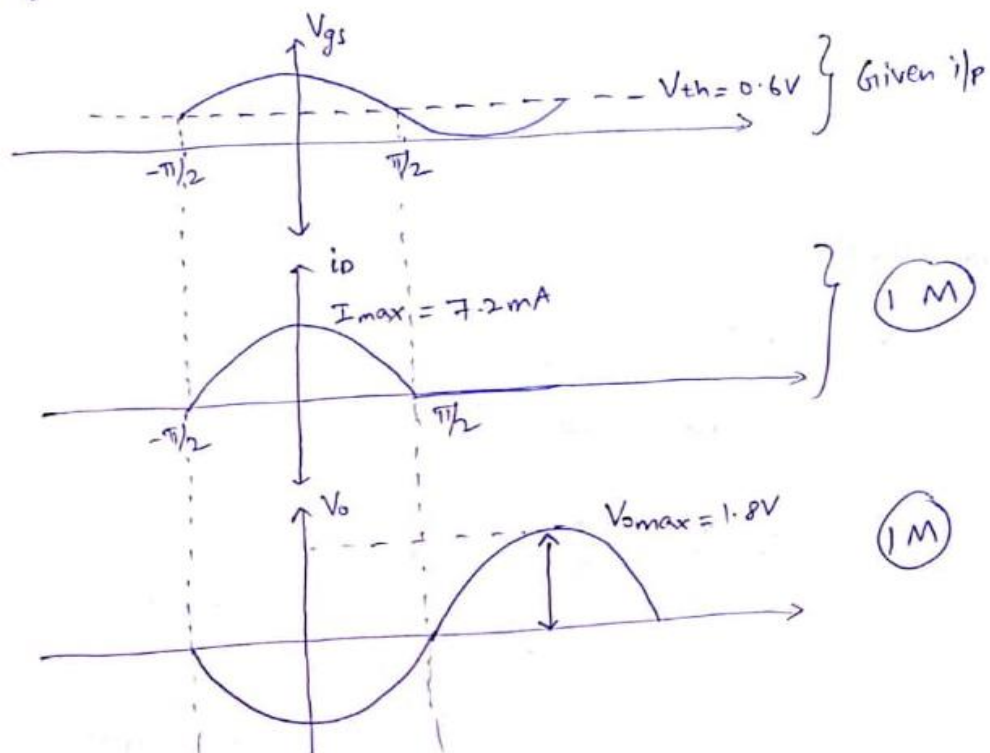

Class B P.A -

Assume: $V_{GS} = V_{th} = 0.6V$

$$V_{dsat} = V_{GS} + V_{gsmax} - V_t = 0.2V$$

The maximum output voltage: $V_{o_{max}} \approx V_{DD} = 1.8V$

Load Resistance = $R_{Load} = \frac{V_{o_{max}}^2}{2 \cdot P_o}$ [Given $P_o = 5.12W$]

$\therefore R_{Load} = 500\Omega$

Amplitude of fundamental component of Drain current -

$$I_L = \frac{V_{o_{max}}}{R_{Load}} = \frac{1.8}{500} = 3.6 \text{ mA}$$

$$I_{PC} = \frac{2}{\pi} \cdot I_L = \frac{2}{\pi} \times 3.6 \text{ mA} = 2.3 \text{ mA}$$

\therefore Max. Drain current: $I_{max} = \pi \cdot I_{PC} = 7.2 \text{ mA}$

To calculate (W/L)

$$\frac{W}{L} = \frac{2 \times I_{\max}}{\mu_{n\text{cox}} V_{\text{sat}}^2} = 1800$$

(1M)

To calculate L, C

Given: f, BW

$$\therefore Q = \frac{f}{BW} = \frac{2.45 \times 10^9}{500 \times 10^6} = 4.9$$

$$\therefore X_L = X_C = \frac{R}{Q} = \frac{500}{4.9} \approx 102$$

$$\therefore L = \frac{102}{\omega_c} = \frac{102}{2\pi \times 2.45 \times 10^9} = 6.62 \text{ nH} \quad (1M)$$

$$C = \frac{1}{102 \times 2\pi \times 2.45 \times 10^9} = 0.636 \text{ pF} \quad (1M)$$

Q7. A hilbert transform of a signal $m(t) \leftrightarrow m_H(t)$ with the relation : $m_H(t) = \frac{1}{\pi} \int_{-\infty}^{\infty} \frac{m(\tau)}{t-\tau} d\tau$

and the Fourier Transform relation: $M_H(f) = -j \text{sgn}(f) M(f)$

Show that for a upper sideband modulated signal resulting from $m(t)$ and $\cos(2\pi f_c t)$ is given by : $s(t) = \frac{1}{2} [m(t) \cos(2\pi f_c t) - m_H(t) \sin(2\pi f_c t)]$ (2M)

Solution:

$$s(t) = \frac{1}{2}[m(t) \cos(2\pi f_c t) - m_H(t) \sin(2\pi f_c t)]$$

Applying Fourier transform to the above equation, we get

$$S(f) = \frac{1}{4}[M(f - f_c) + M(f + f_c)] - \frac{1}{4j}[M_H(f - f_c) - M_H(f + f_c)]$$

From the definition of Hilbert Transform, we have

$$M_H(f) = -j \operatorname{sgn}(f)M(f)$$

where $\operatorname{sgn}(f)$ is the signum function. Equivalently, we may write

$$\frac{-1}{j}M_H(f - f_c) = \operatorname{sgn}(f - f_c)M(f - f_c) \quad \frac{-1}{j}M_H(f + f_c) = \operatorname{sgn}(f + f_c)M(f + f_c)$$

From the definition of signum function, we note the following for $f > 0$ and $f > f_c$

$$\operatorname{sgn}(f - f_c) = \operatorname{sgn}(f + f_c) = 1$$

Correspondingly, the equation for $S(f)$ reduces to,

$$S(f) = \frac{1}{4}[M(f - f_c) + M(f + f_c)] + \frac{1}{4}[M(f - f_c) - M(f + f_c)] = \frac{1}{2}M(f - f_c)$$

In words, the above result means that, except for a scaling factor, the spectrum of the modulated signal $s(t)$ is the same as that of a DSB-SC modulated signal for $f > f_c$.

For $f > 0$ and $f < f_c$, we have

$$\operatorname{sgn}(f - f_c) = -1 \operatorname{sgn}(f + f_c) = 1$$


Correspondingly, $S(f)$ reduces to,

$$S(f) = \frac{1}{4}[M(f - f_c) + M(f + f_c)] + \frac{1}{4}[-M(f - f_c) - M(f + f_c)] = 0$$



In words, for $f < f_c$, the modulated signal $s(t)$ is zero.


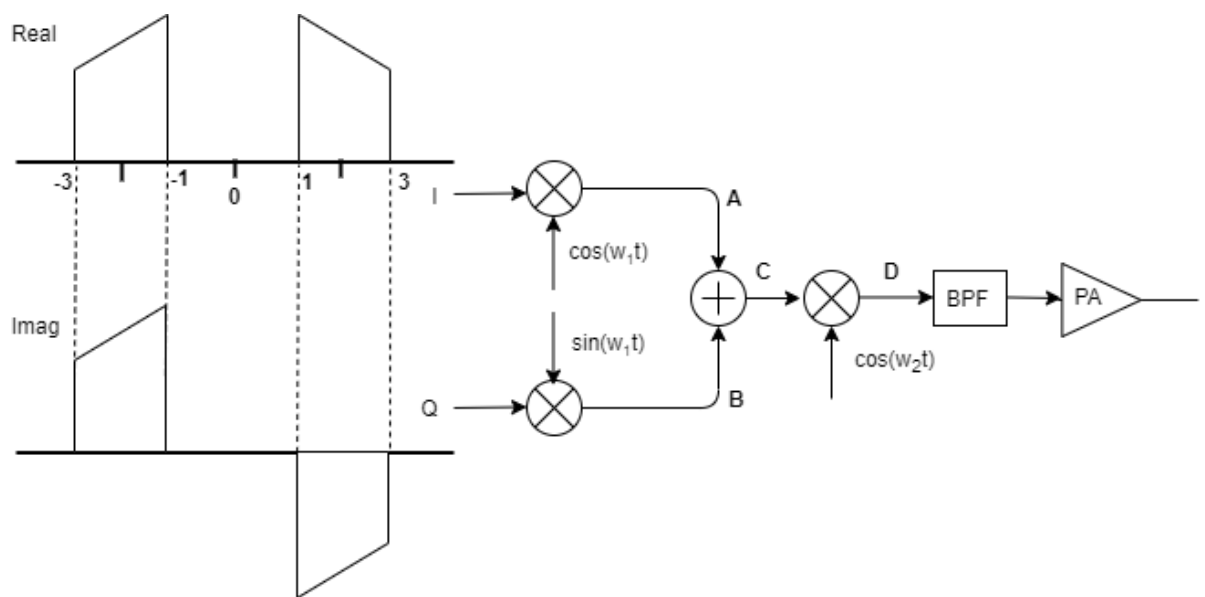
Q8. The below figure shows the concept of Heterodyne Transmitter. Signal conversion happens in two steps as shown. The frequency of up-conversion is $f_0=5\text{GHz}$. Units in spectrum are in MHz. Assume that $f_1=1\text{GHz}$ and $f_2=4\text{GHz}$. The spectrum of I signal is real. The Q spectrum is 90 degrees phase shifted version of I spectrum (Imaginary). The I and Q signals are at base band(Close to DC). Our goal is to have final PA transmitter spectrum at 5GHz.

- Draw the 3D spectrum at A,B,C, and D (4M)
- Sketch the characteristics of the desired BPF?(Center frequency & Stopband) (2M)



Solution:

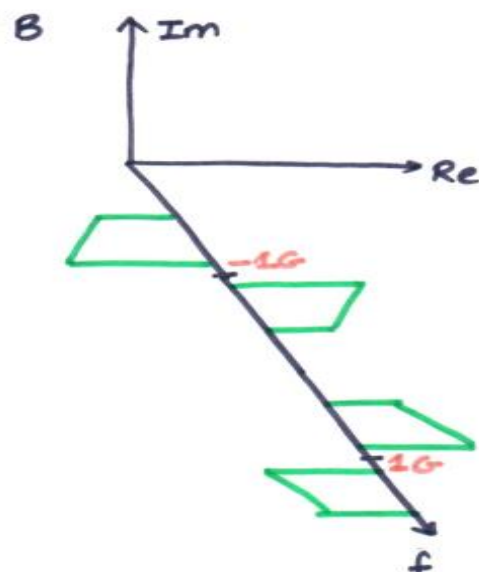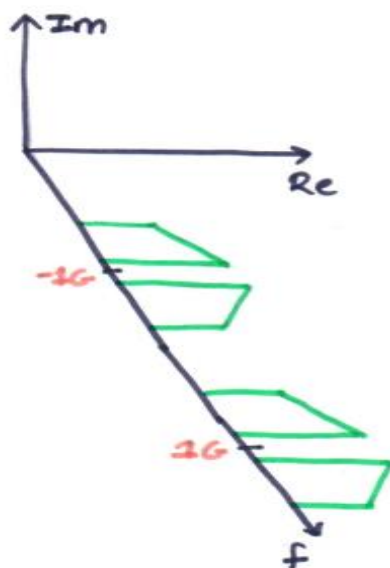

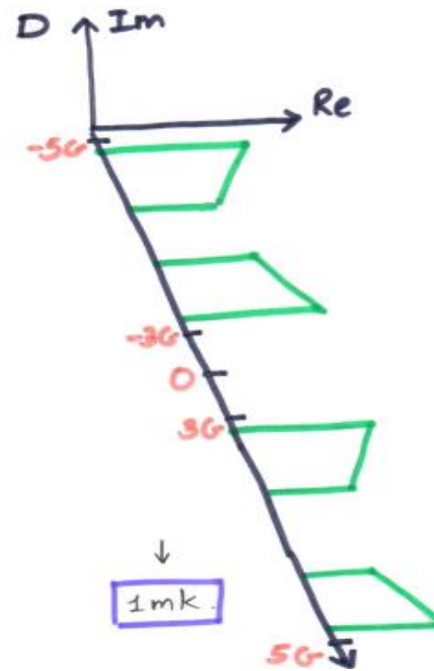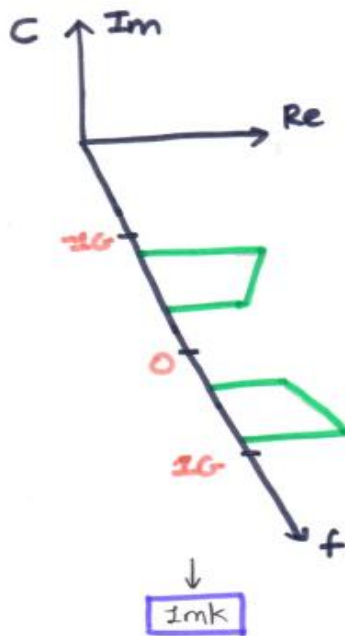

Bandpass characteristics.

As seen in spectrum of D, in addition to the required band at 5GHz, we also have sidebands at 3GHz.

centre frequency = 5GHz - 2 MHz

stopband region =

↓
should reject the
sideband at 3GHz.

specifically make sure that the 3GHz sideband is
cancelled

